

### Question 1.

- (a) (1) What is the **metric prefix** for ten to the power of **fifteen**? (2) What is its **name**?
- (b) Define (1) **precision** and (2) **resolution**.
- (c) A **Wheatstone** bridge has  $R_1 = 600\Omega$ ,  $R_2 = 100\Omega$ ,  $R_3$  as the *variable* resistance, and  $R_X$  as the *unknown* resistance.  $R_3$  varies from  $300\Omega$  to  $3\text{ k}\Omega$ .
- (1) *Draw* the bridge.
  - (2) *Calculate* the range of values of the *unknown* resistance that the bridge can measure.

### Question 2.

- (a) *Name* the kind of **AC bridge** suitable for measuring **low-Q** inductors.
- (b) (1) *Draw* a simple **non-inverting** amplifier's circuit. (2) *Derive* the expression for its voltage **gain**.
- (c) For each of the following properties, in your **script-book** write "**yes**" or "**no**" as to whether a **real** op-amp has that property.
- (1) infinite open loop gain.
  - (2) non-zero output impedance.
  - (3) infinite bandwidth.
  - (4) infinite output impedance.
  - (5) non-zero noise generation.
- (d) *Draw* the circuit for an **op-amp integrator**.

### Question 3.

- (a) When making measurements of a patient's heart during **cardiac surgery**, is it better to *ground* the *sensor*, or not? Justify your answer.
- (b) A simple op-amp **comparator** has a  $1\text{ k}\Omega$  **feedback** resistor and a  $1\text{ k}\Omega$  resistor between its **positive** input and ground. Its minimum and maximum **output** voltages are  $0\text{ V}$  and  $5\text{ V}$ .
- (1) *Draw* the comparator.
  - (2) *Calculate* its minimum and maximum **input** voltages.

### Question 4.

- (a) What is the *unit* of **voltage drift**?
- (b) *Describe* the **Peltier** effect.
- (c) *State* the **sampling theorem**.

### Question 5.

- (a) In a **CRO**, what is the *purpose* of the **graticule lines**?
- (b) **Semiconductor temperature transducers** contain two identical transistors for which the difference in their base-emitter voltages depends on temperature.

(1) Write the formula for that difference voltage  $\Delta V_{be}$  in terms of temperature  $T$ , Boltzmann's constant  $k$ , the electron charge  $q$ , and the two transistors' emitter currents  $I_1$  and  $I_2$ .

(2) Calculate the value of  $\Delta V_{be}$  at a temperature of 300 K, if the emitter currents are 2 mA and 6 mA.

### Question 6.

- (a) Draw a **five-bit synchronous** counter.
- (b) What **advantage** does a *synchronous* counter have over a *ripple* counter?
- (c) Sketch the distorted waveform that results from feeding a *square* wave to a **band** pass filter.

### Question 7.

- (a) If a **DAC** has a *minimum* voltage of 0 volts, a *maximum* voltage of 10.20 volts, and a *resolution* of 40 millivolts, then how many **bits** does it have?
- (b) What is one potential *disadvantage* of a **flash ADC**?
- (c) Draw the *diagram* from the lecture notes for a **ramp ADC**.

### Question 8.

- (a) Define the **common mode rejection ratio** of a differential amplifier.
- (b) A **fluid pressure** transducer with a sensitivity of  $2 \mu\text{V/V/mmHg}$  is excited by a +10 V dc source. Calculate the *output voltage* if a pressure of 50 mmHg is applied.
- (c) Draw the block diagram for an **RF signal generator**.

### Question 9.

- (a) Draw the block diagram for a **spectrum analyser**.
- (b) Why is the interior of a **microwave oven** enclosed in a *metal-wire mesh*?
- (c) List two (2) indoor sources of **capacitive** interference.

**Question 10.**

- (a) The **GPIB** standard defines four (4) classes of device or instrument.
- (1) Name the classes.
  - (2) Give an example for each class.
- (b) In measurements on untuned amplifiers, what is **slew rate**?
- (c) *Draw* the circuit diagram for a **Wien** oscillator.