

### Question 1.

(a) Given one example each of:

- (i) a **direct**,
- (ii) an **indirect**, and
- (iii) a **null** measurement.

(b) Name the types of **AC bridge** suitable for measuring:


- (i) High-Q inductors?
- (ii) Capacitance?
- (iii) Low-Q inductors?
- (iv) A wide range of Q values?

(c) If a **thermistor** has a resistance of  $R_0 = 300 \text{ k}\Omega$  at the reference temperature  $T_0 = 300 \text{ K}$  (kelvin), and a temperature coefficient  $\beta = 4000 \text{ K}$ , then at what **temperature**  $T$  is its resistance  $R = 280 \text{ k}\Omega$ ? (*Hint: see formula sheet.*)

### Question 2.


(a) What are five (5) properties of an **ideal** operational amplifier?

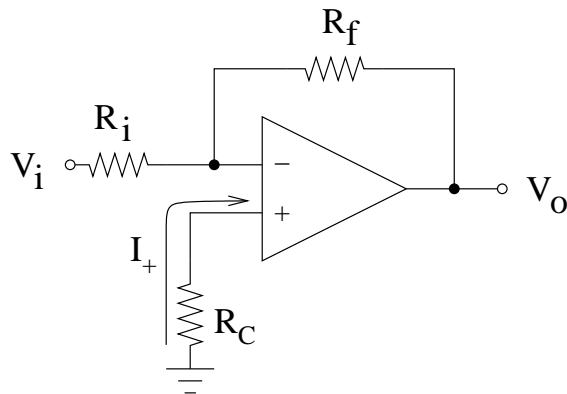(b) The following circuit involves a **real** op-amp.




- (i) What does the **compensation resistor** compensate for?
- (ii) Given that  $R_i = 3 \text{ k}\Omega$  and  $R_f = 6 \text{ k}\Omega$ , what is a suitable value for  $R_C$ ?

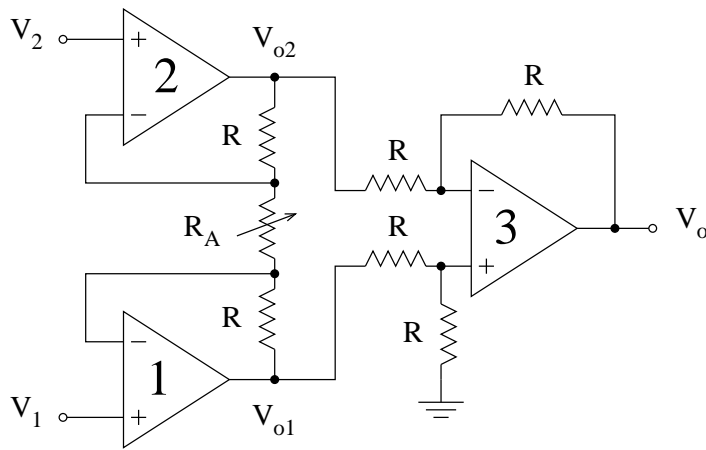(c) The following is a design for an instrumentation amplifier.




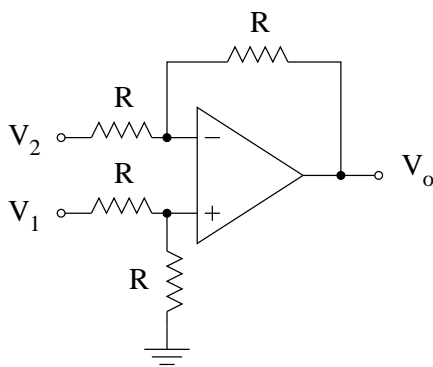What are its **advantages** over the following simpler design?



### Question 3.

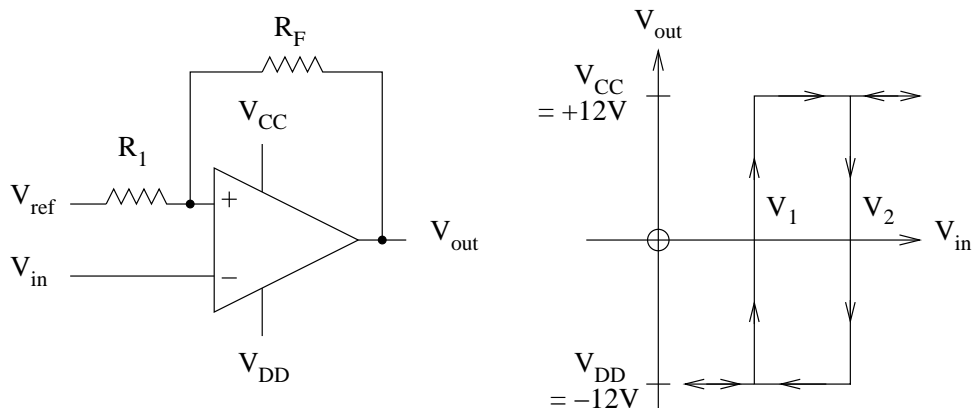- (a) For the simple Schmitt trigger in the next diagram, assume that the maximum and minimum output voltages are +12V and -12V, that  $R_1 = 3 \text{ k}\Omega$  and  $R_F = 6 \text{ k}\Omega$ , and that  $V_{\text{ref}} = 2 \text{ V}$ .




**Calculate** the input voltages  $V_1$  and  $V_2$  at which the transitions occur.

- (b) A *ten-bit* (10-bit) Digital to Analog Converter (DAC) has a minimum output voltage of zero volts (for the binary input zero) and a maximum output voltage of 10.23 V. What **binary number** produces the output voltage 4.32 V?
- (c) Compare the average speeds of these three types of Analog to Digital Converter as functions of  $n$  (the number of bits of output).

- (i) Ramp ADC.
- (ii) Successive Approximation ADC.
- (iii) Flash ADC.

**Question 4.**

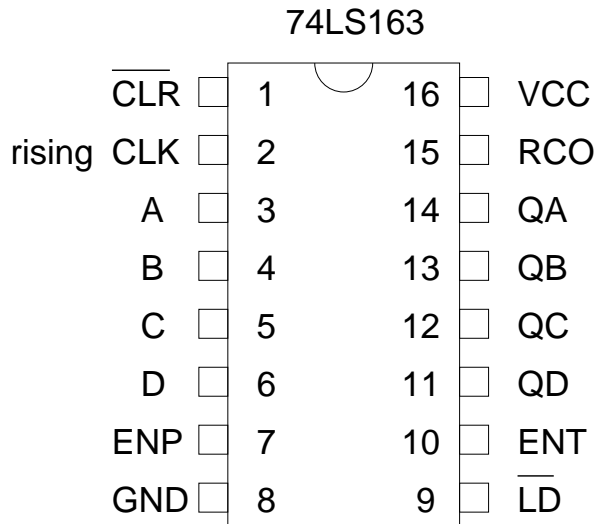(a) A 74LS163 counter has the following pinout diagram,




Using a 74LS163 and any logic gates that may be required, **design** a counter that produces the repeating sequence 0, . . . , 9.

- (b) Give three (3) advantages of **automated test equipment** (ATE).
- (c) For the **general purpose interface bus** (GPIB):
  - (i) What are the four (4) kinds of devices in the GPIB?
  - (ii) Of which two (2) types of devices does a minimal GPIB system consist?
  - (iii) What are the three (3) functions of a **controller**?
  - (iv) Give the two (2) GPIB data rates, in kilobytes per second.

**Question 5.**

(a) Here is an oscillator circuit:

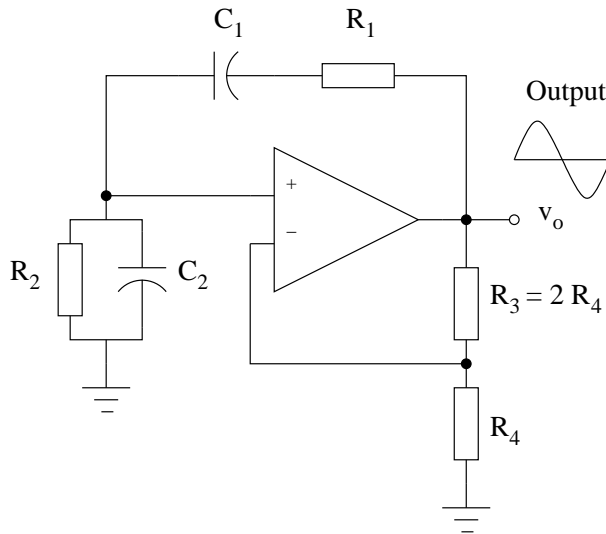

What type of oscillator is it?

(b) For a pulse waveform, define the following terms:

- (i) Rise Time,
- (ii) Pulse Width,
- (iii) Overshoot,
- (iv) Ringing.

(c) In the operation of a frequency counter, describe the role of each of these four signals:

- (i) Time Base output,
- (ii) Reset,
- (iii) Strobe,
- (iv) Main Gate Flip-Flop output.

**Question 6.**

(a) **Draw** the *time-base* waveform produced by a **sweep generator**. **Label** each of the *sections* and *significant points* of the waveform.


(b) Suppose a CRO has an input impedance of  $1\text{ M}\Omega$  in parallel with  $30\text{ pF}$ , and is connected to  $90\text{ cm}$  of coaxial cable (with a capacitance of  $100\text{ pF}$  per metre) to a signal generator producing a  $1\text{ MHz}$  sine wave.

- (i) Draw an **equivalent circuit** (using resistors and capacitors) for the signal generator, coaxial cable, and CRO input.
- (ii) What is the **capacitive impedance** of the combination of CRO input and cable?
- (iii) If the signal generator has a source impedance of  $560\Omega$ , then what is the **ratio** of the voltage measured by the CRO *divided by* the signal generator's Thevenin voltage?

(c) What is a **voltage controlled oscillator (VCO)**?

**Question 7.**

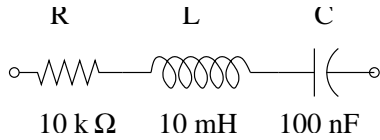- (a) Define **total harmonic distortion** (THD).
- (b) **Calculate** the total (complex) **impedance** of this RLC series resonant tank circuit at an angular frequency of 1000 radians per second:



- (c) In a **tuned transformer**, there is a magnetic coupling between the primary and secondary windings.
- (i) If this coupling is large, what effect does it have on the Q of the circuit?
- (ii) What happens to the shape of the frequency response curve if the coupling is very large?

**Question 8.**

- (a) What is the **effective thermal noise bandwidth**  $\Delta f$  of a 1 kΩ resistor with 5 V<sub>rms</sub> across its terminals at a temperature of 300 K? (*Hint*: see formula sheet.)
- (b) **Electrically** coupled interference voltage increases with what four (4) quantities?
- (c) If an **electric shield** has an opening in the shape of a cylinder with a diameter of 2 cm and a sleeve of length 8 cm, then what is the **attenuation** of an interference waveform of wavelength 60 cm that enters that opening? (*Hint*: see formula sheet.)

## Formulas

$$0^{\circ}\text{C} = 273 \text{ K}$$

$$k = 1.38 \times 10^{-23} \text{ W / Hz / K}$$

$$\text{Attenuation} = 54.5 (L/\lambda_c) \sqrt{1 - (\lambda_c/\lambda)^2}, \text{ where } \lambda_c = \pi r$$

$$P = 4kT \cdot \Delta f$$

$$v_{\text{RMS}}^2 = PR$$