

# Discrete Maths - Digital Logic

## Laboratory 3: Full Adder

### **Assessment Criteria**


Assessment in this lab is based on these performance measures:

1. Mastery of Boolean Logic;
2. Adherence to Design Principles;
3. Circuit construction;
4. Record of Results;
5. Tidying up after yourself.



### **1 Equipment List**

1. 5V power supply
2. Protoboard
3. Switch and LED board
4. Cutters
5. Pliers
6. Single strand hook-up wire
7. One 74LS08 (quad AND)
8. One 74LS86 (quad XOR)


## 74LS04 HEX NOT

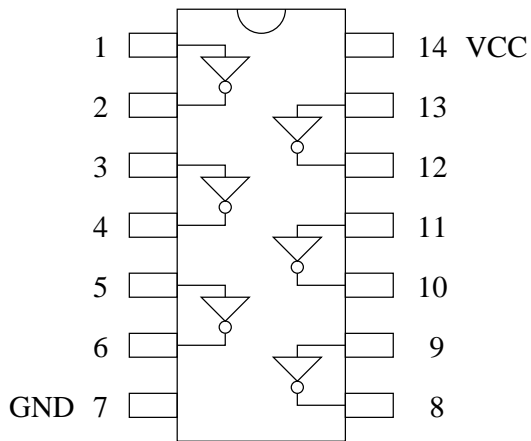

## 74LS08 QUAD AND

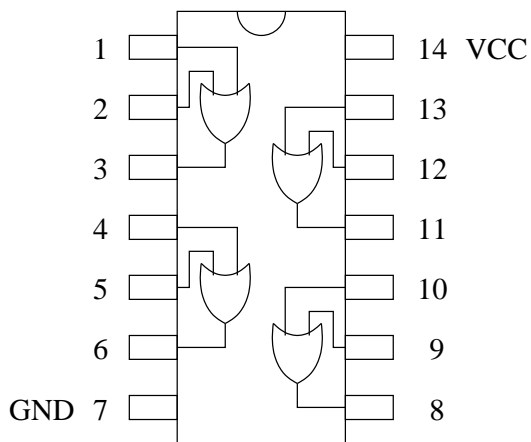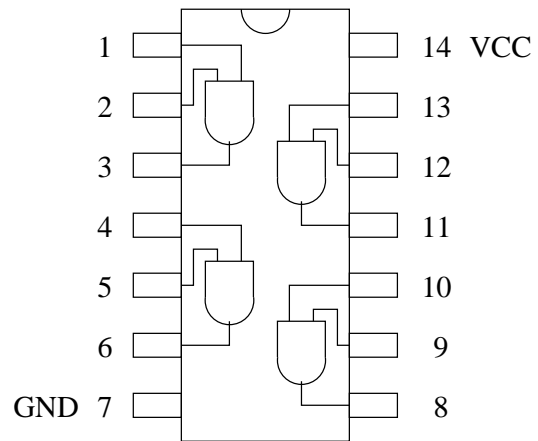



## 74LS32 QUAD OR

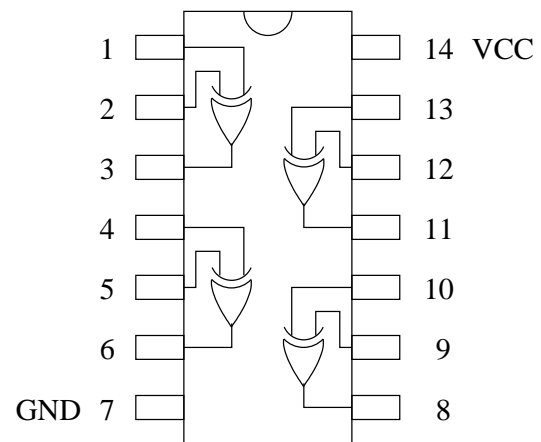

## 74LS86 QUAD XOR
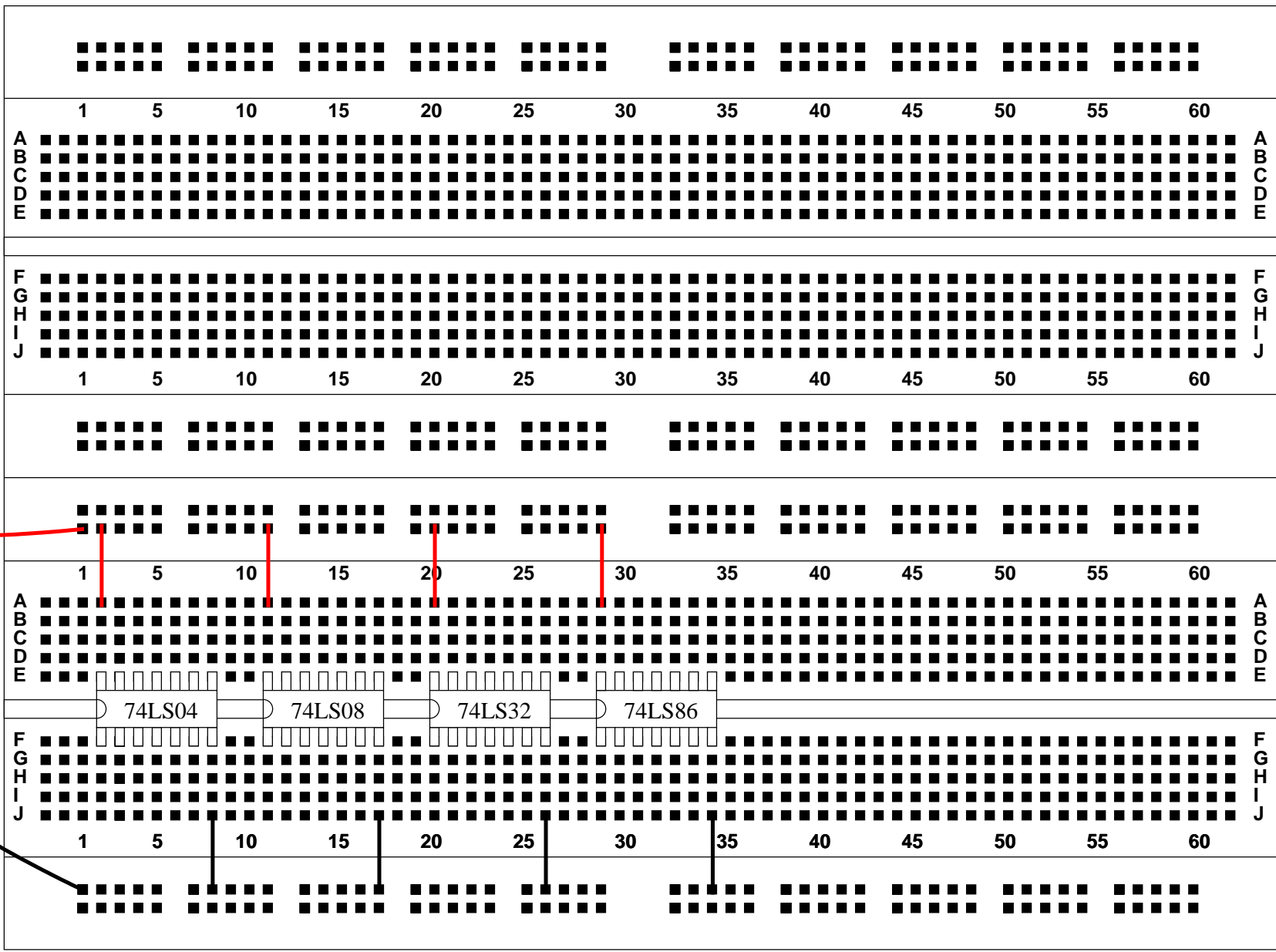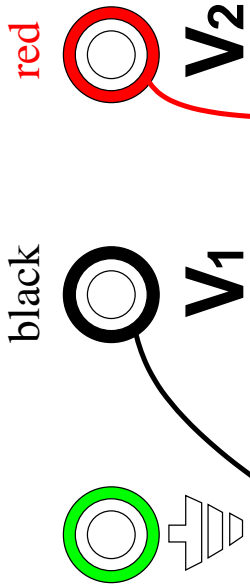
# Project Boards

**K<sub>A</sub>N<sub>D</sub>H** Model  
**GL-24**



## 2 Full Adder

The *Half Adder* (HA) of the previous laboratory produces a Carry-Out, but has *no* Carry-In, so it can **only** be used to add **1-bit** numbers. In manual decimal arithmetic, each digit is added separately, starting from the least significant digit, and the carry-out from each digit is forwarded as an input to the next higher digit. Similarly, an  $n$ -bit **binary addition** can be implemented by **cascading**  $n$  *Full Adders*. **Each** Full Adder has **three (3) input bits** named **A**, **B** and Carry-In  $C_i$ , which it adds together; and **two (2) output bits** named Carry-Out ( $C_o$ ) and Sum ( $S$ ) (which together form a **two-bit** number). **Complete the following Truth Table for a Full Adder, then have it checked and marked by a demonstrator.**

*Hint 1:*  $0 + 0 + 1 = 1$ . That has carry out = 0, and sum = 1. Hence, what is **1** as a **2-bit** number?

*Hint 2:*  $1 + 1 + 1 = 3$ . How is **3** represented in binary? (You **NEED** to know the binary numbers up to at least **15**, otherwise how will you complete your MAT1DM exam?)

A	B	$C_i$	$C_o$	S
0	0	0	<b>0</b>	<b>0</b>
0	0	1		
0	1	0	<b>0</b>	<b>1</b>
0	1	1		
1	0	0	<b>0</b>	<b>1</b>
1	0	1		
1	1	0	<b>1</b>	<b>0</b>
1	1	1		

In the table, those **output** values for  $C_o$  and  $S$  that are printed in **bold italic** have a carry **input**  $C_i$  equal to 0. This ( $C_i = 0$ ) corresponds to the output of a Half Adder. **In the next space, prove this fact mathematically, then have your answer checked and marked by a demonstrator.**

*Hint:* The formula for a **half adder** is  $H = A + B$ , and a **full adder** has  $F = A + B + C_i$ .


Observe that the **S** bit is **1** whenever there are an **odd** number of ones among the inputs  $A$ ,  $B$  and  $C_i$ . That means that **S** is the **XOR** of the three inputs:  $S = A \oplus B \oplus C_i$ . We can implement that as two XORs in series.

Also note that  $C_o$  is 1 whenever **at least two** of the inputs are 1. We could implement that using three AND gates and an OR, so that the Full Adder would use six gates altogether, but there's a more efficient solution.

Since  $F = A + B + C_i = (A + B) + C_i$  one Half Adder can do the  $A + B$  part of the addition, as noted above. We can use a second HA to add  $C_i$  to get the full adder's sum bit  $S$ . How to obtain its carry-out bit  $C_o$ ? On a moment's reflection,  $C_o = 1$  when either HA has a carry-out. So one might consider using an OR gate to generate  $C_o$ .

*But can both* Half Adders produce a carry at the *same time*? The first HA produces a carry  $C1 = 1$  when both  $A$  and  $B$  are 1, and then its sum  $S1 = 0$  and the second HA's carry bit  $C2 = 0$ . Therefore the OR gate can be replaced by an **XOR**, so **two (2) ICs** suffice, a **74LS08** quad AND and a **74LS86** quad XOR.

Switch

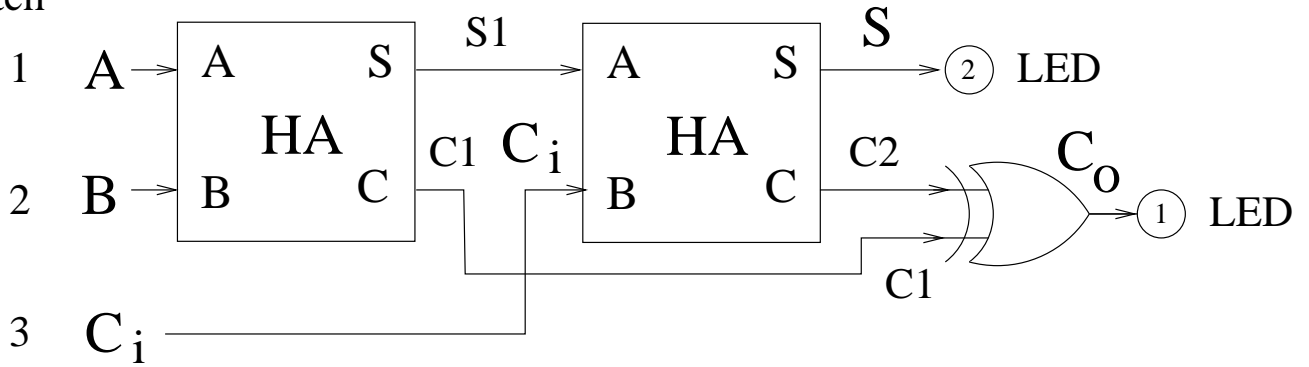

There are 8 signals: **3 inputs** A, B and  $C_i$  to connect to switches; **3 intermediate signals** S1, C1, C2; and **2 outputs**  $C_o$  and S, to be connected to LEDs. Fill out the following signal/switch/LED/color table. Remember: **one color for each signal; one signal for each color.**

Signal	Switch	LED	Color
A		none	
B		none	
$C_i$		none	
S1	none	none	
C1	none	none	
C2	none	none	
$C_o$	none		
S	none		

**This table MUST be approved and MARKED by a demonstrator before you can proceed.**

**Draw** the full design of this circuit, using two AND gates and three XOR gates, in the space provided. You **MUST number all pins**, not only in this diagram, but in every logic diagram in these labs. You also also **MUST** record the **switch** numbers, **LED** numbers, and wire **colors** on the logic diagram.

**DO NOT build anything yet!**



**This design MUST be approved and MARKED by a demonstrator before you can proceed.**

**Abiding by the approved color coding scheme**, you may now build the full adder circuit, using one 74LS08 and one 74LS86.

The demonstrators will **NOT** diagnose — much less repair — faults in a circuit that is not wisely color-coded, because it's unreasonable to expect anyone to spend disproportionate time on fixing someone else's poorly constructed circuit.

**You have been warned.** So build each circuit sensibly.

**Have your circuit construction checked and MARKED by a demonstrator.**


Test the full adder, and record its observed outputs in the following truth table.

1	2	3	$I$	2
A	B	$C_i$	$C_o$	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

**These results absolutely MUST be checked and MARKED by a demonstrator before you proceed.**
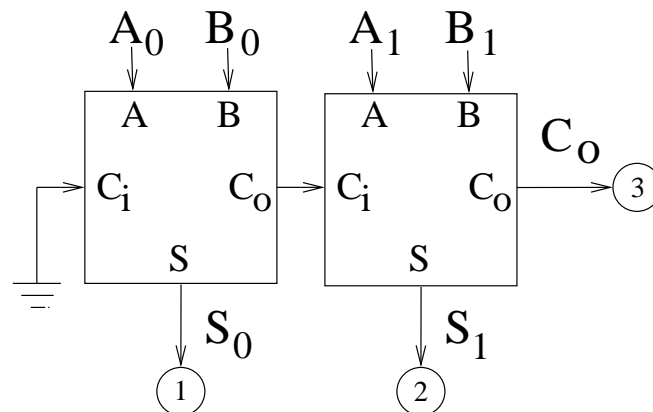
### 3 Two-Bit Adder

A two-bit adder can be constructed from two full adders, by *joining a wire* from the carry-out of one full adder to the carry-in of the other. Be careful to *remove* the wire that was used to connect a switch to the second full adder's Carry-In. **Combine your full adder with that of a neighboring group to construct this circuit:**



**You MUST get the 2-bit adder construction checked and MARKED by a demonstrator before proceeding.**

Test the two-bit adder, and record the observed results in the next truth table. (Warning: Pay close attention to the order of the bits.)

1	2	1	2	3	2	1
$A_1$	$B_1$	$A_0$	$B_0$	$C_0$	$S_1$	$S_0$
0	0	0	0			
0	0	0	1			
0	0	1	0			
0	0	1	1			
0	1	0	0			
0	1	0	1			
0	1	1	0			
0	1	1	1			
1	0	0	0			
1	0	0	1			
1	0	1	0			
1	0	1	1			
1	1	0	0			
1	1	0	1			
1	1	1	0			
1	1	1	1			

*These results MUST be checked and MARKED by a demonstrator, so keep the circuit INTACT until you have the mark for it.*

## 4 Clean Up

**LEAVE** all **equipment** (board, components, and tools) **on your bench**.

Please **return** every **cord** to the racks, every **wire** to the recycle bin.

**Clean** the bench **and the carpet**, and place your **chair under the bench**.

Have your **clean-up checked and SIGNED for by a demonstrator**.

**Hand in your completion sheet**.

2007 Sep 14 Fri 12:24 Geoffrey Tobin